

# Microwave Resonators


S.M. Riazul Islam, PhD

University of Dhaka

# Microwave Resonators

- Applications
  - Filters
  - Oscillators
  - Frequency Meters
  - Tuned Amplifiers
- Similar to RLC resonators!

# Series/Parallel Resonant Circuit

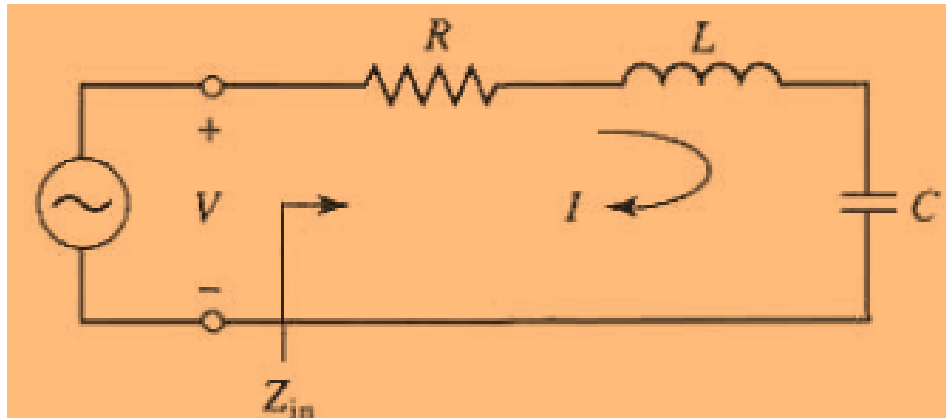

$$Z_{in} = R + j\omega L - j\frac{1}{\omega C},$$

$$P_{in} = \frac{1}{2} V I^* = \frac{1}{2} Z_{in} |I|^2 = \frac{1}{2} Z_{in} \left| \frac{V}{Z_{in}} \right|^2$$

$$= \frac{1}{2} |I|^2 \left( R + j\omega L - j\frac{1}{\omega C} \right).$$

The power dissipated by the resistor,  $R$ , is

$$P_{loss} = \frac{1}{2} |I|^2 R,$$

the average magnetic energy stored in the inductor,  $L$ , is

$$W_m = \frac{1}{4} |I|^2 L,$$

and the average electric energy stored in the capacitor,  $C$ , is

$$W_e = \frac{1}{4} |V_c|^2 C = \frac{1}{4} |I|^2 \frac{1}{\omega^2 C},$$

$$P_{in} = P_{loss} + 2j\omega(W_m - W_e)$$

$$Z_{in} = \frac{2P_{in}}{|I|^2} = \frac{P_{loss} + 2j\omega(W_m - W_e)}{\frac{1}{2}|I|^2}.$$

$$Z_{in} = \frac{P_{loss}}{\frac{1}{2}|I|^2} = R,$$

$$\omega_0 = \frac{1}{\sqrt{LC}}.$$

# Series/Parallel Resonant Circuit

$$Q = \omega \frac{\text{(average energy stored)}}{\text{(energy loss/second)}} \\ = \omega \frac{W_m + W_e}{P_l}$$

Q, measure of the loss of a resonant circuit!

$$Q = \omega_0 \frac{2W_m}{P_{\text{loss}}} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Behavior of the I/P Impedance at resonance:

$\omega = \omega_0 + \Delta\omega$ , where  $\Delta\omega$  is small

$$Z_{\text{in}} = R + j\omega L \left( 1 - \frac{1}{\omega^2 LC} \right) \\ = R + j\omega L \left( \frac{\omega^2 - \omega_0^2}{\omega^2} \right)$$

since  $\omega_0^2 = 1/LC$ . Now  $\omega^2 - \omega_0^2 = (\omega - \omega_0)(\omega + \omega_0) = \Delta\omega(2\omega - \Delta\omega) \simeq 2\omega\Delta\omega$  for small  $\Delta\omega$ . Thus,

$$Z_{\text{in}} \simeq R + j2L\Delta\omega \\ \simeq R + j \frac{2RQ\Delta\omega}{\omega_0}$$

An useful form for distributed element resonators!

# Series/Parallel Resonant Circuit

Resonator with loss can be modeled as lossless resonator whose resonant frequency has been replaced with a complex effective resonant frequency:

$$\omega_0 \leftarrow \omega_0 \left(1 + \frac{j}{2Q}\right)$$

$$Z_{\text{in}} = j2L(\omega - \omega_0).$$

$$\begin{aligned} Z_{\text{in}} &= j2L \left( \omega - \omega_0 - j\frac{\omega_0}{2Q} \right) \\ &= \frac{\omega_0 L}{Q} + j2L(\omega - \omega_0) = R + j2L\Delta\omega, \end{aligned}$$


Half-Power BW:

$$|Z_{\text{in}}|^2 = 2R^2$$



$$\Delta\omega/\omega_0 = \text{BW}/2$$

$$|R + jRQ(\text{BW})|^2 = 2R^2$$

$$\text{BW} = \frac{1}{Q}.$$

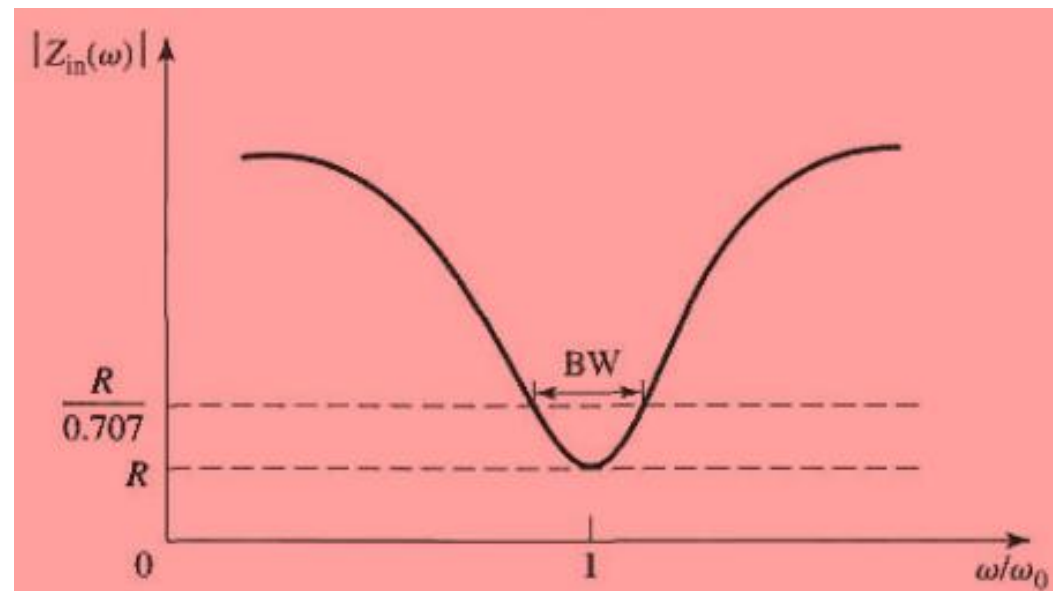

# Series/Parallel Resonant Circuit

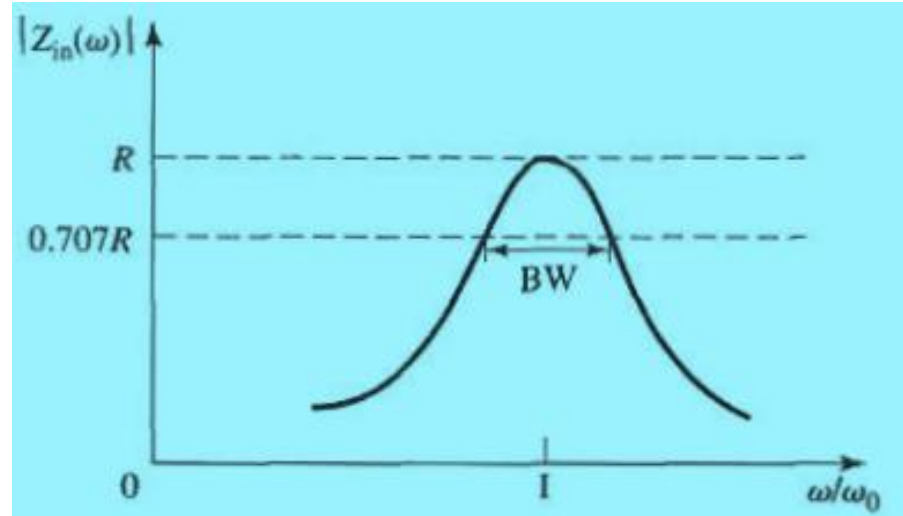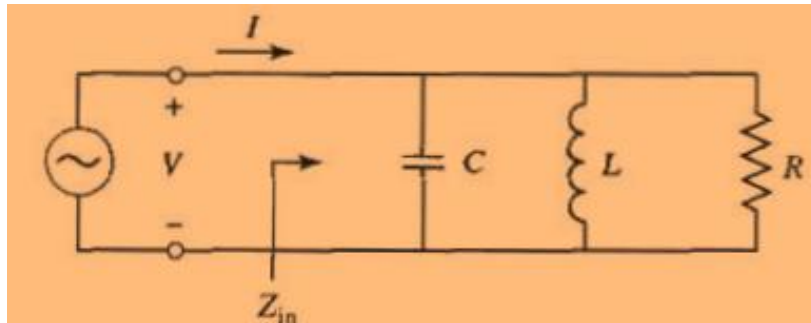

$$Z_{in} = \left( \frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right)^{-1}$$

$$\begin{aligned} P_{in} &= \frac{1}{2} V I^* = \frac{1}{2} Z_{in} |I|^2 = \frac{1}{2} |V|^2 \frac{1}{Z_{in}^*} \\ &= \frac{1}{2} |V|^2 \left( \frac{1}{R} + \frac{j}{\omega L} - j\omega C \right). \end{aligned}$$

$$P_{loss} = \frac{1}{2} \frac{|V|^2}{R},$$

$$W_e = \frac{1}{4} |V|^2 C,$$

$$W_m = \frac{1}{4} |I_L|^2 L = \frac{1}{4} |V|^2 \frac{1}{\omega^2 L},$$

$$P_{in} = P_{loss} + 2j\omega(W_m - W_e),$$

$$Z_{in} = \frac{2P_{in}}{|I|^2} = \frac{P_{loss} + 2j\omega(W_m - W_e)}{\frac{1}{2}|I|^2},$$

$$Z_{in} = \frac{P_{loss}}{\frac{1}{2}|I|^2} = R,$$

$$\omega_0 = \frac{1}{\sqrt{LC}},$$

# Series/Parallel Resonant Circuit

$$Q = \omega_0 \frac{2W_m}{P_{\text{loss}}} = \frac{R}{\omega_0 L} = \omega_0 RC,$$

$$\frac{1}{1+x} \simeq 1 - x + \dots$$

Letting  $\omega = \omega_0 + \Delta\omega$ , where  $\Delta\omega$  is small, (6.12) can be rewritten as

$$Z_{\text{in}} \simeq \left( \frac{1}{R} + \frac{1 - \Delta\omega/\omega_0}{j\omega_0 L} + j\omega_0 C + j\Delta\omega C \right)^{-1}$$


$$\simeq \left( \frac{1}{R} + j \frac{\Delta\omega}{\omega_0^2 L} + j\Delta\omega C \right)^{-1}$$

$$\simeq \left( \frac{1}{R} + 2j\Delta\omega C \right)^{-1}$$

$$\simeq \frac{R}{1 + 2j\Delta\omega RC} = \frac{R}{1 + 2jQ\Delta\omega/\omega_0}$$

# Series/Parallel Resonant Circuit

- Loaded and Unloaded Q

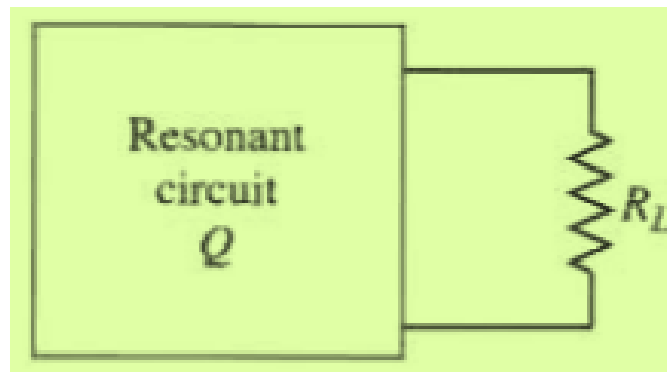

$$Q_e = \begin{cases} \frac{\omega_0 L}{R_L} & \text{for series circuits} \\ \frac{R_L}{\omega_0 L} & \text{for parallel circuits,} \end{cases}$$

$$\frac{1}{Q_L} = \frac{1}{Q_e} + \frac{1}{Q}$$




# Series/Parallel Resonant Circuit

Quantity	Series Resonator	Parallel Resonator
Input Impedance/admittance	$Z_{in} = R + j\omega L - j\frac{1}{\omega C}$ $\simeq R + j\frac{2RQ\Delta\omega}{\omega_0}$	$Y_{in} = \frac{1}{R} + j\omega C - j\frac{1}{\omega L}$ $\simeq \frac{1}{R} + j\frac{2Q\Delta\omega}{R\omega_0}$
Power loss	$P_{loss} = \frac{1}{2} I ^2 R$	$P_{loss} = \frac{1}{2}\frac{ V ^2}{R}$
Stored magnetic energy	$W_m = \frac{1}{4} I ^2 L$	$W_m = \frac{1}{4} V ^2 \frac{1}{\omega^2 L}$
Stored electric energy	$W_e = \frac{1}{4} I ^2 \frac{1}{\omega^2 C}$	$W_e = \frac{1}{4} V ^2 C$
Resonant frequency	$\omega_0 = \frac{1}{\sqrt{LC}}$	$\omega_0 = \frac{1}{\sqrt{LC}}$
Unloaded $Q$	$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$	$Q = \omega_0 RC = \frac{R}{\omega_0 L}$
External $Q$	$Q_e = \frac{\omega_0 L}{R_L}$	$Q_e = \frac{R_L}{\omega_0 L}$

# Transmission Line Resonators
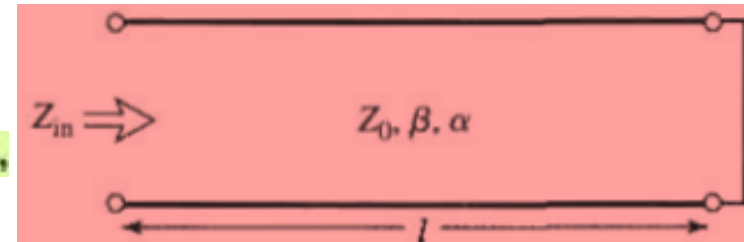
## Short-Circuited $\lambda/2$ Line

At the frequency  $\omega = \omega_0$ , the length of the line is  $\ell = \lambda/2$ ,



$$Z_{in} = Z_0 \tanh(\alpha + j\beta)\ell.$$

Using an identity for the hyperbolic tangent gives

$$Z_{in} = Z_0 \frac{\tanh \alpha \ell + j \tan \beta \ell}{1 + j \tan \beta \ell \tanh \alpha \ell}$$

Observe that  $Z_{in} = jZ_0 \tan \beta \ell$  if  $\alpha = 0$  (no loss).

$$\tan \beta \ell = \tan \left( \pi + \frac{\Delta \omega \pi}{\omega_0} \right) = \tan \frac{\Delta \omega \pi}{\omega_0} \simeq \frac{\Delta \omega \pi}{\omega_0}.$$

$$Z_{in} \simeq Z_0 \frac{\alpha \ell + j(\Delta \omega \pi / \omega_0)}{1 + j(\Delta \omega \pi / \omega_0) \alpha \ell} \simeq Z_0 \left( \alpha \ell + j \frac{\Delta \omega \pi}{\omega_0} \right),$$

Now let  $\omega = \omega_0 + \Delta \omega$ ,

$$\beta \ell = \frac{\omega \ell}{v_p} = \frac{\omega_0 \ell}{v_p} + \frac{\Delta \omega \ell}{v_p}$$

Since  $\ell = \lambda/2 = \pi v_p / \omega_0$

$$\beta \ell = \pi + \frac{\Delta \omega \pi}{\omega_0},$$

since  $\Delta \omega \alpha \ell / \omega_0 \ll 1$

# Transmission Line Resonators

$$Z_0 \left( \alpha \ell + j \frac{\Delta \omega \pi}{\omega_0} \right),$$


$$Z_{\text{in}} = R + 2jL\Delta\omega,$$

$$R = Z_0\alpha\ell,$$

$$L = \frac{Z_0\pi}{2\omega_0}.$$

$$C = \frac{1}{\omega_0^2 L}.$$

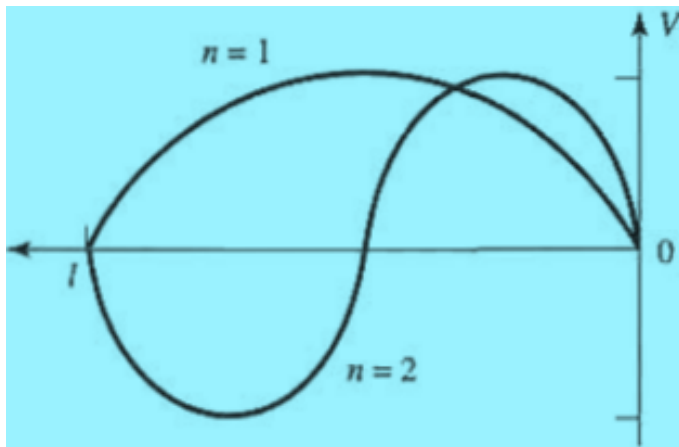Resonance also occurs for  $\ell = n\lambda/2, n = 1, 2, 3, \dots$



$$Q = \frac{\omega_0 L}{R} = \frac{\pi}{2\alpha\ell} = \frac{\beta}{2\alpha},$$

since  $\beta\ell = \pi$  at the first resonance.

# Transmission Line Resonators

## Short-Circuited $\lambda/4$ Line

Now assume that  $\ell = \lambda/4$  at  $\omega = \omega_0$ , and let  $\omega = \omega_0 + \Delta\omega$ .

$$\beta\ell = \frac{\omega_0\ell}{v_p} + \frac{\Delta\omega\ell}{v_p} = \frac{\pi}{2} + \frac{\pi\Delta\omega}{2\omega_0},$$

$$\cot\beta\ell = \cot\left(\frac{\pi}{2} + \frac{\pi\Delta\omega}{2\omega_0}\right) = -\tan\frac{\pi\Delta\omega}{2\omega_0} \simeq \frac{-\pi\Delta\omega}{2\omega_0},$$

$$\begin{aligned} Z_{\text{in}} &= Z_0 \tanh(\alpha + j\beta)\ell \\ &= Z_0 \frac{\tanh\alpha\ell + j\tan\beta\ell}{1 + j\tan\beta\ell\tanh\alpha\ell} \\ &= Z_0 \frac{1 - j\tanh\alpha\ell\cot\beta\ell}{\tanh\alpha\ell - j\cot\beta\ell}, \end{aligned}$$

$$Z_{\text{in}} = Z_0 \frac{1 + j\alpha\ell\pi\Delta\omega/2\omega_0}{\alpha\ell + j\pi\Delta\omega/2\omega_0} \simeq \frac{Z_0}{\alpha\ell + j\pi\Delta\omega/2\omega_0},$$

since  $\alpha\ell\pi\Delta\omega/2\omega_0 \ll 1$

$$Z_{\text{in}} = \frac{1}{(1/R) + 2j\Delta\omega C},$$

$$R = \frac{Z_0}{\alpha\ell}$$

$$C = \frac{\pi}{4\omega_0 Z_0}$$

$$L = \frac{1}{\omega_0^2 C}$$

$$Q = \omega_0 RC = \frac{\pi}{4\alpha\ell} = \frac{\beta}{2\alpha},$$

since  $\ell = \pi/2\beta$  at resonance.

# Transmission Line Resonators

## Open-Circuited $\lambda/2$ Line

The input impedance of an open-circuited line of length  $\ell$  is

$$Z_{\text{in}} = Z_0 \coth(\alpha + j\beta)\ell = Z_0 \frac{1 + j \tan \beta\ell \tanh \alpha\ell}{\tanh \alpha\ell + j \tan \beta\ell}.$$

As before, assume that  $\ell = \lambda/2$  at  $\omega = \omega_0$ , and let  $\omega = \omega_0 + \Delta\omega$ . Then,

$$\beta\ell = \pi + \frac{\pi \Delta\omega}{\omega_0},$$

and so

$$\tan \beta\ell = \tan \frac{\Delta\omega\pi}{\omega} \simeq \frac{\Delta\omega\pi}{\omega_0},$$

and  $\tanh \alpha\ell \simeq \alpha\ell$ . Using these results in (6.32) gives

$$Z_{\text{in}} = \frac{Z_0}{\alpha\ell + j(\Delta\omega\pi/\omega_0)}.$$

$$R = \frac{Z_0}{\alpha\ell},$$

$$C = \frac{\pi}{2\omega_0 Z_0}.$$

$$L = \frac{1}{\omega_0^2 C}.$$


$$Q = \omega_0 RC = \frac{\pi}{2\alpha\ell} = \frac{\beta}{2\alpha},$$

since  $\ell = \pi/\beta$  at resonance.

# Rectangular Waveguide Cavities

- Because of radiation loss from open-ended waveguide, waveguide resonators are usually short circuited at both ends; closed box or cavity.
- Coupling by a small aperture, probe or loop.
- Resonant frequency and Q?

# Cavity Resonator

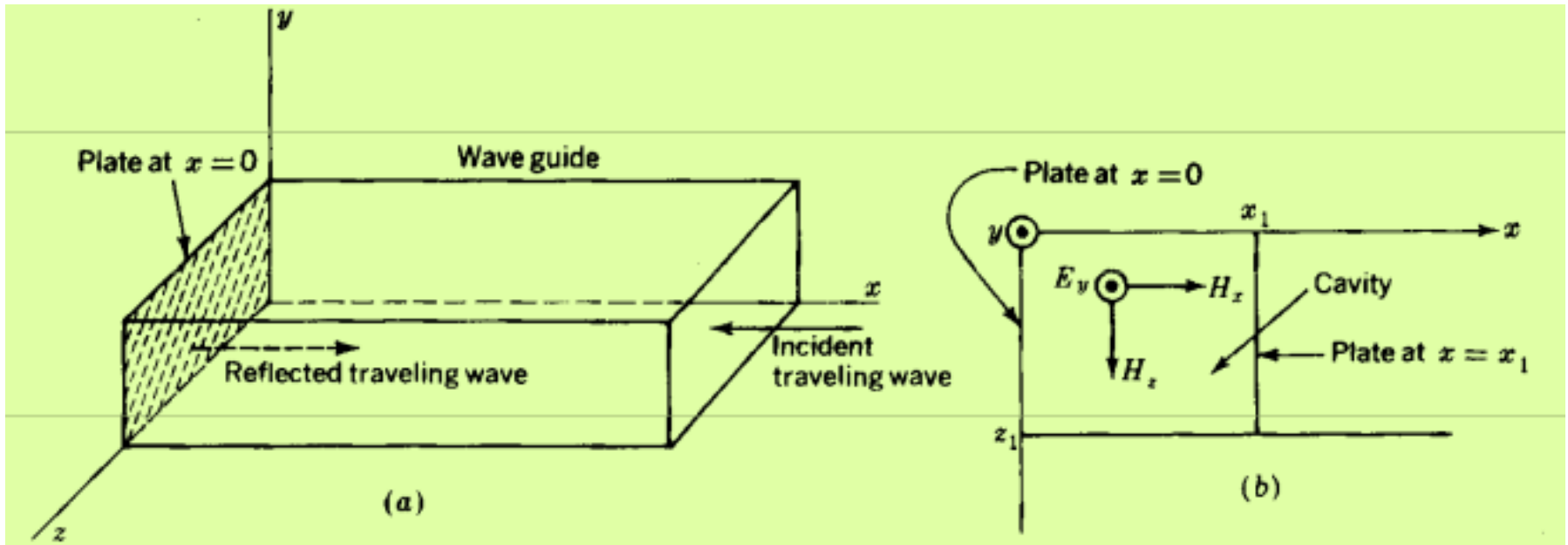

$$E_y = \frac{j\beta Z_{yz}}{k_z} H_0 \sin k_z z e^{j(\omega t \pm \beta x)} \quad (1)$$

$$H_x = H_0 \cos k_z z e^{j(\omega t \pm \beta x)} \quad (2)$$

$$H_z = \frac{j\beta}{k_z} H_0 \sin k_z z e^{j(\omega t \pm \beta x)} \quad (3)$$

$$k_z = m\pi/z_1.$$

# Cavity Resonator

$$E_y = \frac{-j\beta Z_{yz}}{k_z} H_0 \sin k_z z (e^{j\beta x} - e^{-j\beta x}) e^{j\omega t} \quad (4)$$

$$= \frac{2\beta Z_{yz}}{k_z} H_0 \sin k_z z \sin \beta x e^{j\omega t} \quad (5)$$

Inserting another conducting plate across the guide at  $x = x_1$  requires that  $\beta = k_x = l\pi/x_1$ . Noting that the transverse-wave impedance  $Z_{yz} = \omega\mu/\beta = \omega\mu/k_x$ , we get

$$E_y = \frac{2\omega\mu}{k_z} H_0 \sin k_x x \sin k_z z e^{j\omega t} \quad (6)$$

Proceeding in like manner for the magnetic field components, we get

$$H_x = -2H_0 \sin k_x x \cos k_z z e^{j[\omega t + (\pi/2)]} \quad (7)$$

$$H_z = \frac{2k_x}{k_z} H_0 \cos k_x x \sin k_z z e^{j[\omega t + (\pi/2)]} \quad (8)$$



# Cavity Resonator

the designation appropriate to our example would be  $TE_{lm0}$ . Now  $k^2 = k_z^2 = \gamma^2 + \omega^2 \mu \epsilon$ , but  $\gamma^2 = -\beta^2$  ( $\alpha = 0$ ) and  $\beta = k_x$ . Thus,

$$k_z^2 = -k_x^2 + \omega^2 \mu \epsilon = -k_x^2 + (2\pi f)^2 \frac{1}{(f\lambda)^2}$$


so

$$\lambda = \frac{2}{\sqrt{(l/x_1)^2 + (m/z_1)^2}} \quad (9)$$


$TE_{110}$  mode in a square-box resonator ( $x_1 = z_1$ ) is given by

$$\lambda = \frac{2}{\sqrt{2/x_1^2}} = 1.41x_1 \quad (\text{m}) \quad (10)$$


# Cavity Resonator

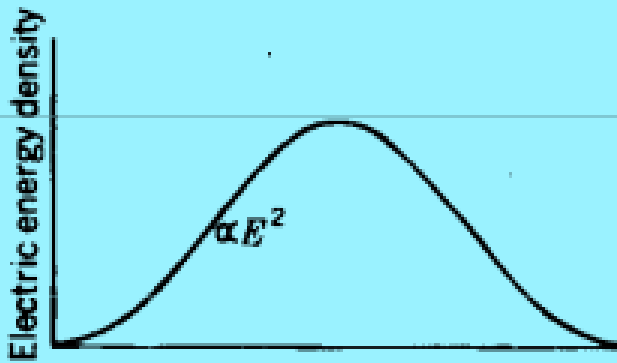

$t = 0$

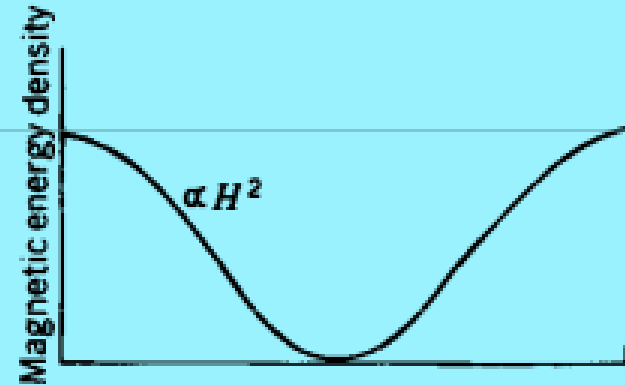

$t = \frac{T}{4}$

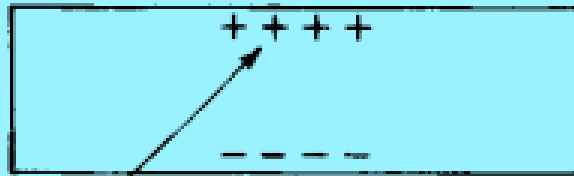

Charges



Currents

# Cavity Resonator

$$Q = 2\pi \frac{\text{total energy stored}}{\text{decrease in energy in 1 cycle}}$$

or

$$Q = \frac{2}{\delta} \frac{\text{volume of cavity}}{\text{interior surface area of cavity}} \quad (18)$$

where  $\delta = 2 \operatorname{Re} Z_c / \omega \mu_0 = 1/e$  depth of penetration. For copper  $\delta = 6.6 \times 10^{-2} / \sqrt{f}$ . If  $x_1 = z_1 = 100$  mm and  $y_1 = 50$  mm, we have that the resonant wavelength  $\lambda = 141$  mm and  $Q = 17,500$  (dimensionless).