



EEE-1222: Basic Electronics

Computer Science & Engineering (CSE)

Lecture PPT # 03

<http://study.riazulislam.com>



University of
Dhaka

APECE
DU

Course Teacher: Dr. S.M. Riazul Islam


Date: 2012 Year, 07 Month, 10 Day



Contents


- Diode characteristics and parameters
- Graphical analysis of diode circuits
- Ideal diode and practical diode
- Rectification
- Diode Logic Circuits
- Diode Clipping and Clamping Circuits
- Power Dissipation

Diode Characteristics and Parameters

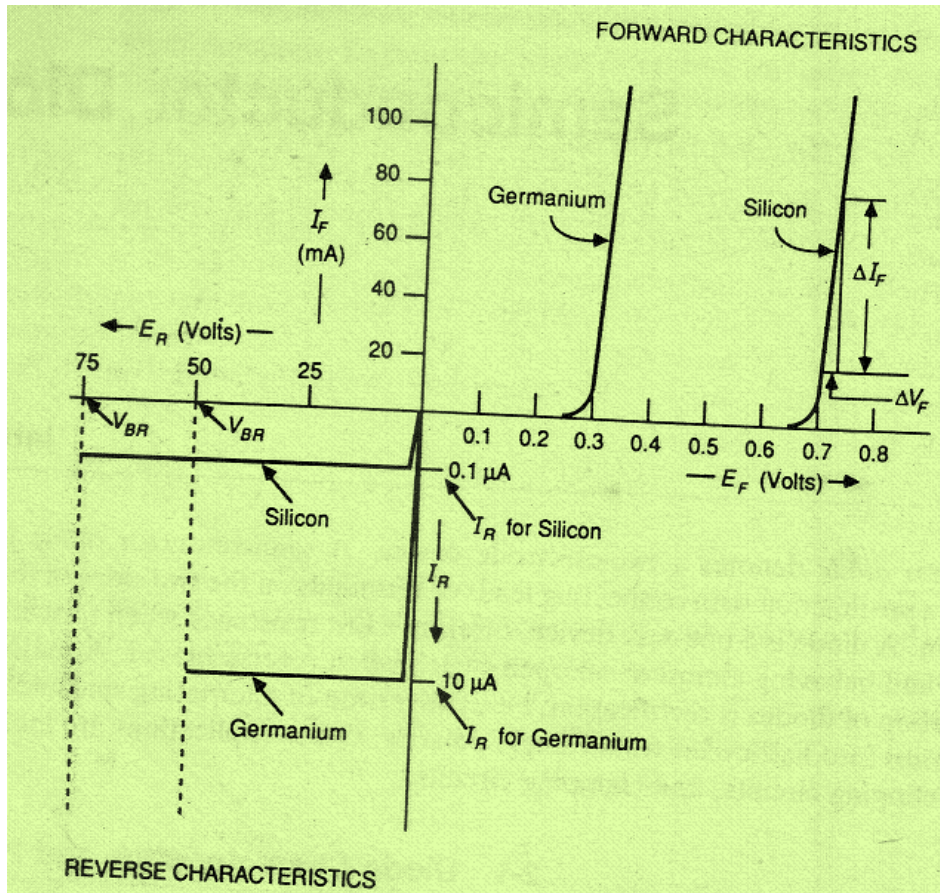


- Forward voltage drop
- Reverse saturation current
- Reverse breakdown voltage
- Dynamic resistance
- Maximum forward current

Diode Characteristics and Parameters

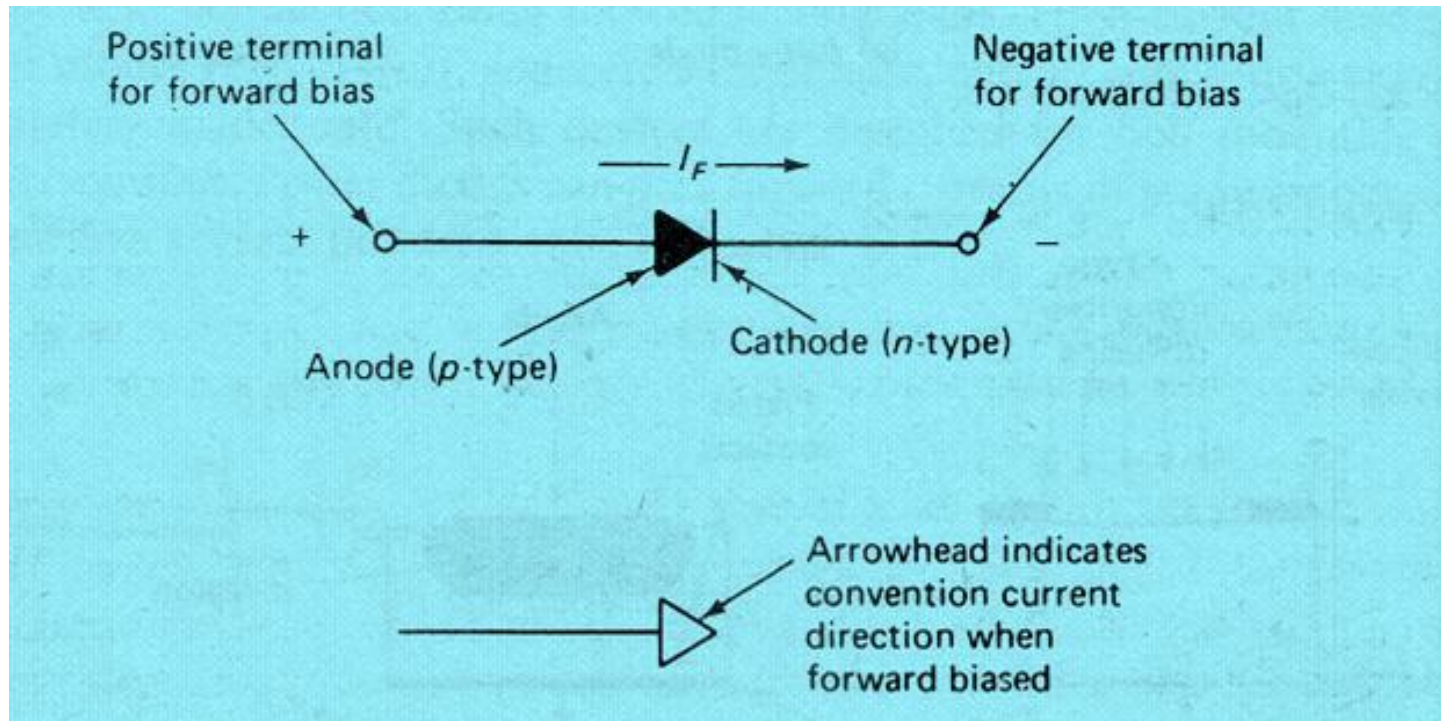

Graphical Analysis of Diode Circuits

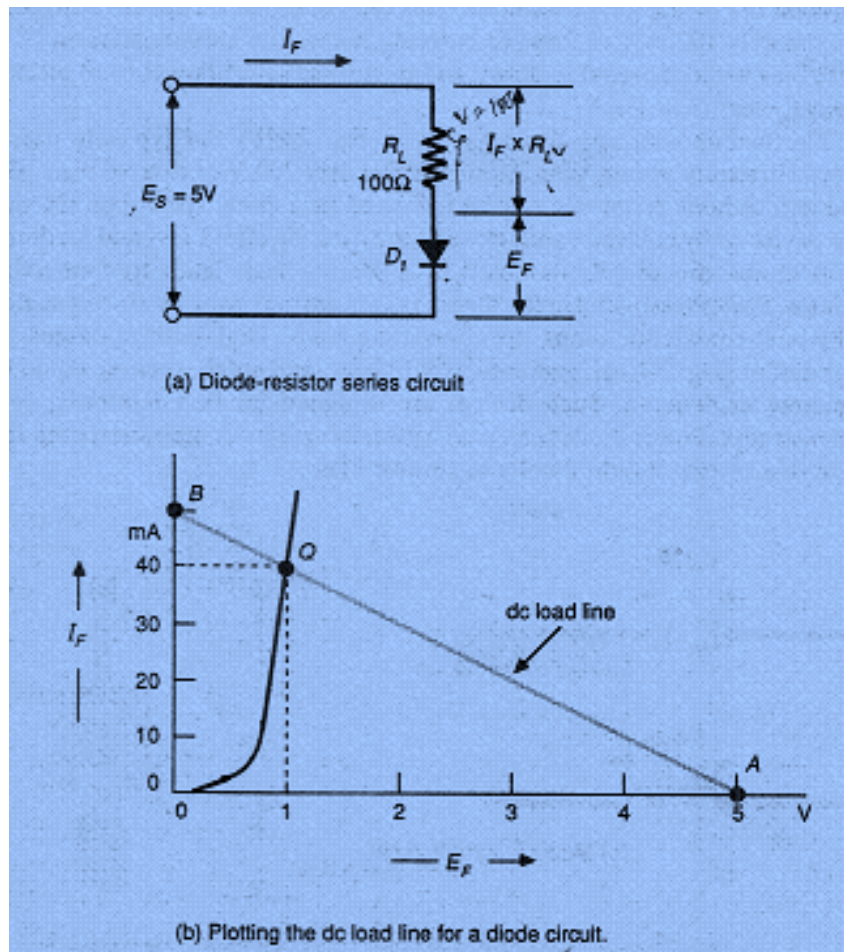

$$E_S = I_F R_L + E_F$$

Graphical Analysis of Diode Circuits

From Eq. 2-1,

$$E_S = I_F R_L + E_F$$

When $I_F = 0$,

$$E_S = 0 + E_F$$

Therefore, the diode voltage is

$$E_F = E_S = 5 \text{ V}$$

Plot point *A* on the diode characteristics at $I_F = 0$ and $E_F = 5 \text{ V}$.

When $E_F = 0$,

$$E_S = I_F R_L + 0$$


or,

$$I_F = \frac{E_S}{R_L}$$

$$= \frac{5 \text{ V}}{100 \Omega} = 50 \text{ mA}$$

Plot point *B* on the diode characteristics at $I_F = 50 \text{ mA}$ and $E_F = 0$. Now draw the dc load line through points *A* and *B*.

Graphical Analysis of Diode Circuits

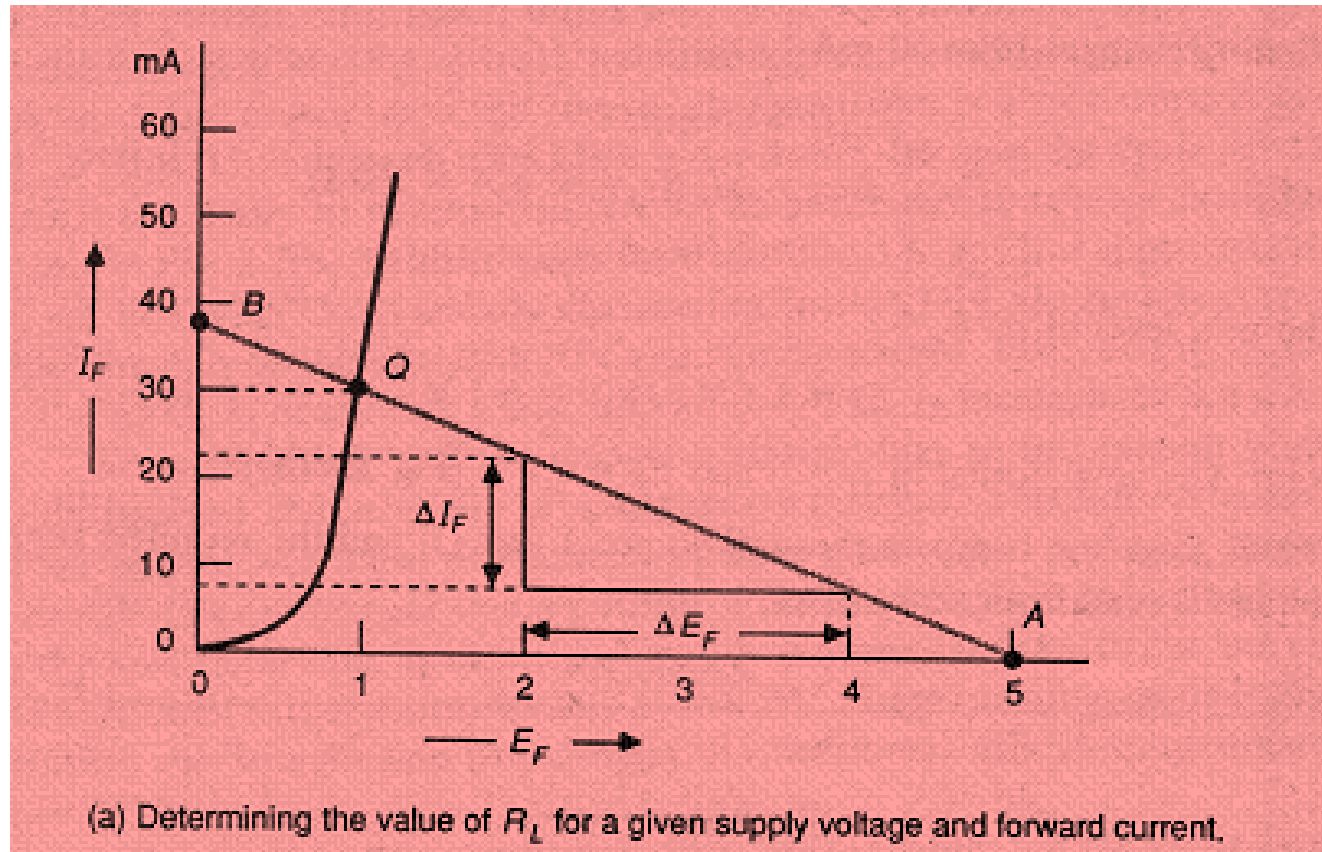

Graphical Analysis of Diode Circuits

Example 2-2 For the circuit shown in Fig. 2-5(a), determine a new value of load resistance which will give a forward current of 30 mA.

Solution

From Eq. 2-1,

$$E_F = E_S - I_F R_L$$

When $I_F = 0$,

$$E_F = E_S = 5 \text{ V}$$


Plot point *A* on the characteristics [Fig. 2-6(a)] at $I_F = 0$ and $E_F = 5 \text{ V}$.

Point *Q* is plotted on the device characteristic at $I_F = 30 \text{ mA}$.

The new dc load line is now drawn through points *A* and *Q*, and R_L is determined as the reciprocal of the slope of the load line.

$$R_L = \frac{\Delta E_F}{\Delta I_F} = \frac{2 \text{ V}}{15 \text{ mA}} = 133 \Omega$$

Ideal Diode and Practical Diode

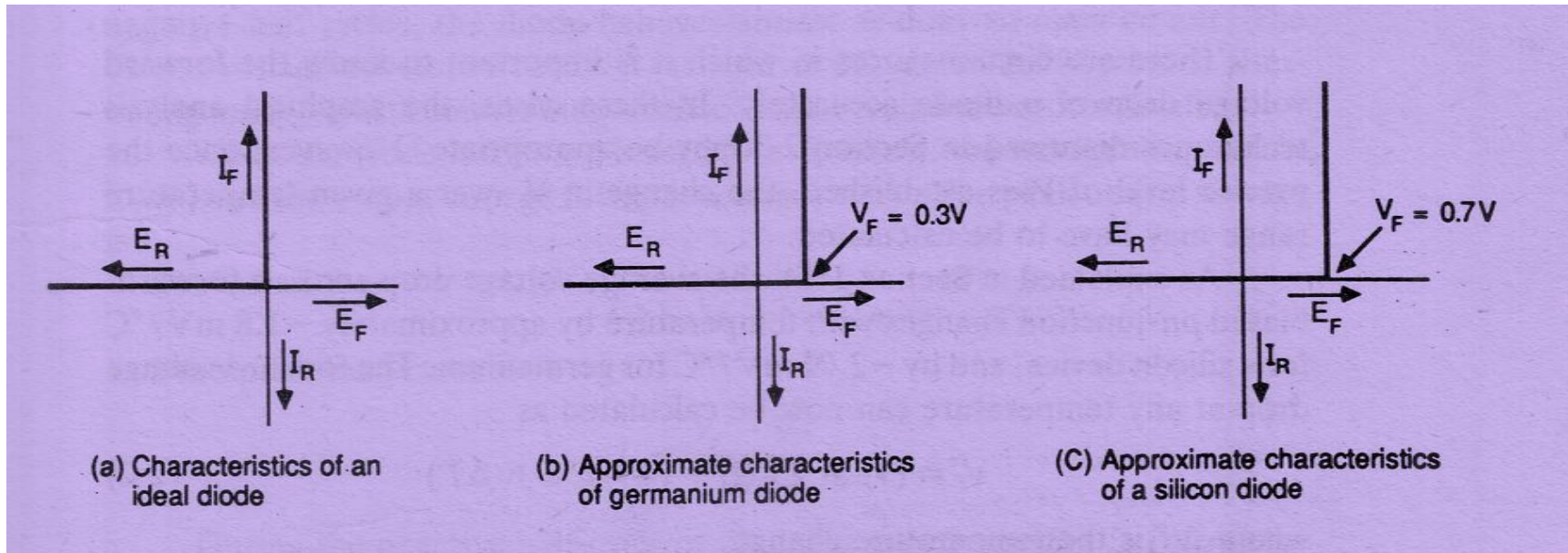

Rectification

Half-Wave Rectification

$$E_P = V_P - V_F \quad (2-3)$$


$$I_P = \frac{V_P - V_F}{R_L} \quad (2-4)$$

In this case the output voltage is

$$E_O = -I_R \times R_L \quad (2-5)$$


Rectification

Half-Wave Rectification

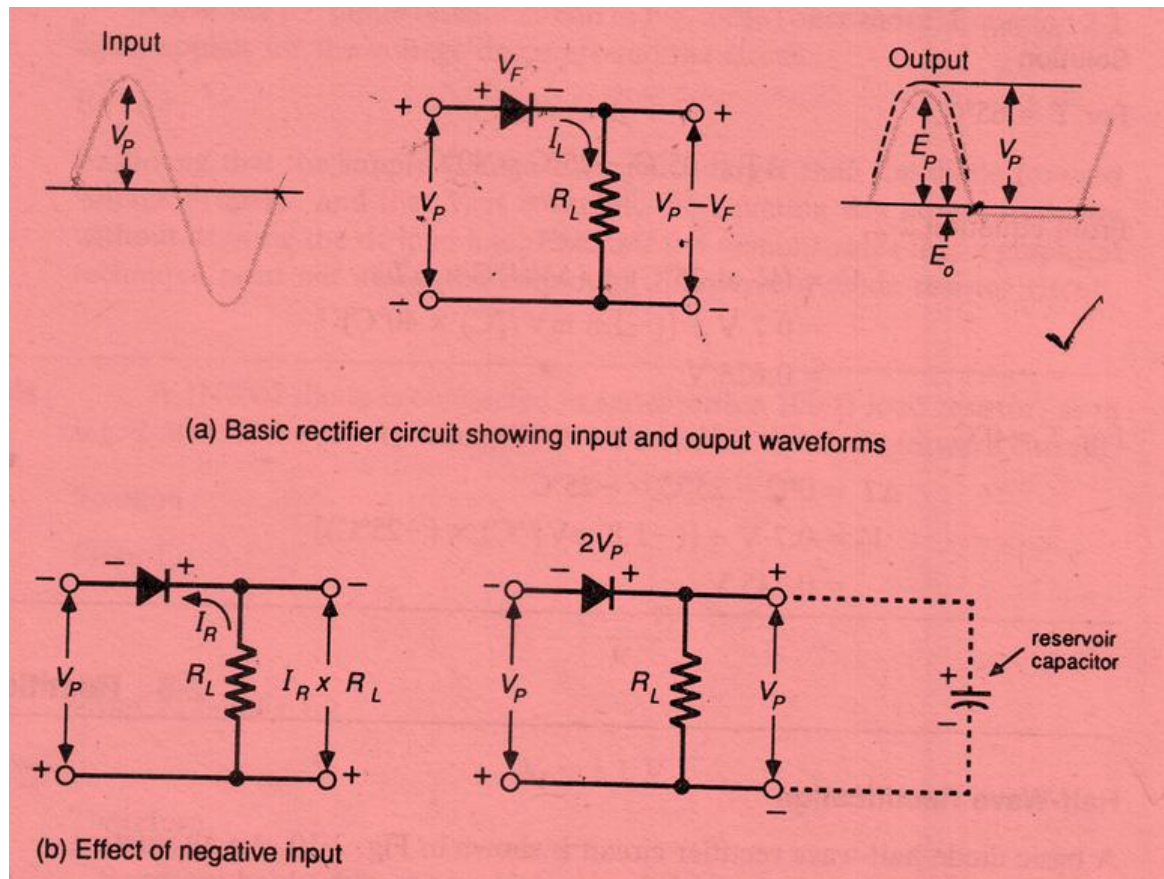

Rectification


Full-Wave Rectification

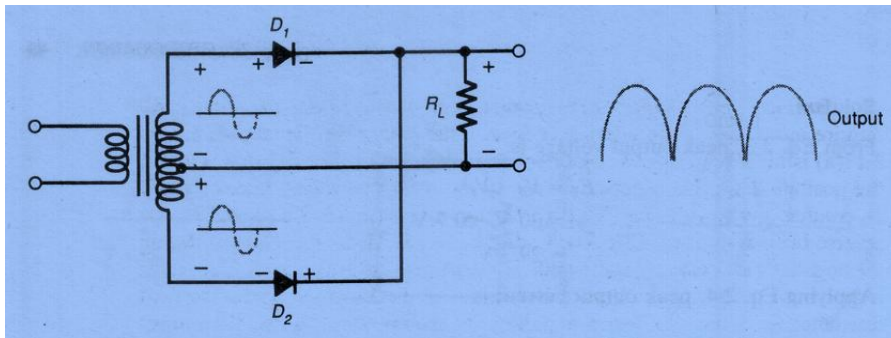

$$E_P = V_P - 2V_F$$

$$V_P = (V_F \text{ for } D_3) + (V_R \text{ for } D_1)$$

$$V_R = V_P - V_F \approx V_P$$

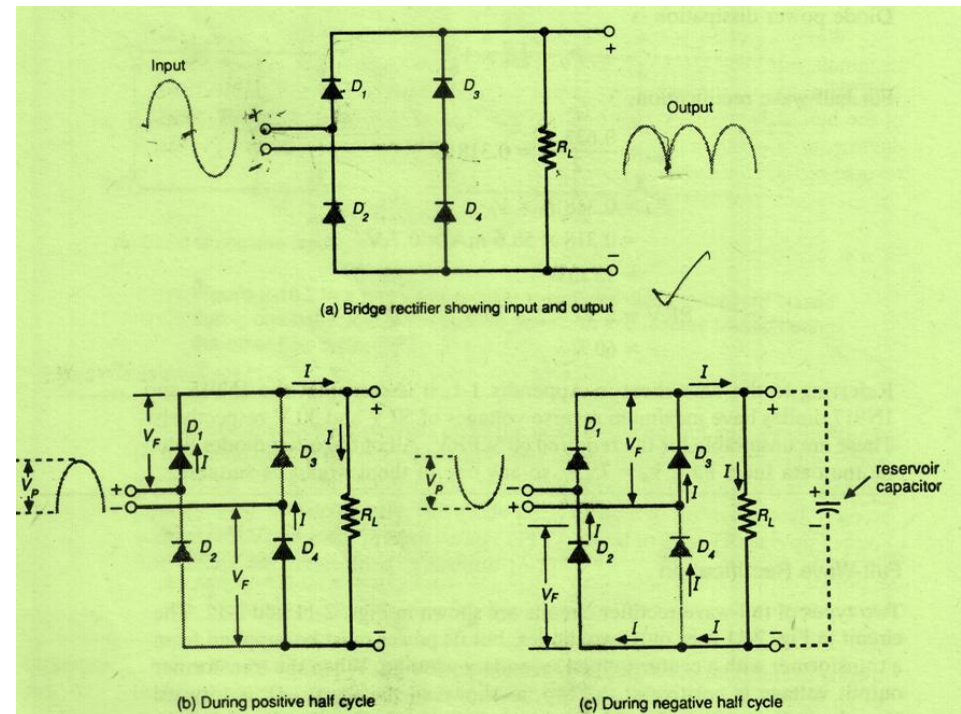

Rectification


A diode with $V_F = 0.7 \text{ V}$ is connected as a half-wave rectifier, as shown in Fig. 2-10. The load resistance is $R_L = 500 \Omega$, and the input voltage has a peak amplitude of 30 V . Calculate the peak positive output voltage, the peak load current, and the diode power dissipation. Also, determine the PRV for the diode, and select a suitable device for the diode.

$$\begin{aligned}E_P &= V_P - V_F \\ &= 30 \text{ V} - 0.7 \text{ V} \\ &= 29.3 \text{ V}\end{aligned}$$

$$I_P = \frac{V_P - V_F}{R_L} = \frac{29.3 \text{ V}}{500 \Omega}$$


Diode Logic Circuits

AND Logic

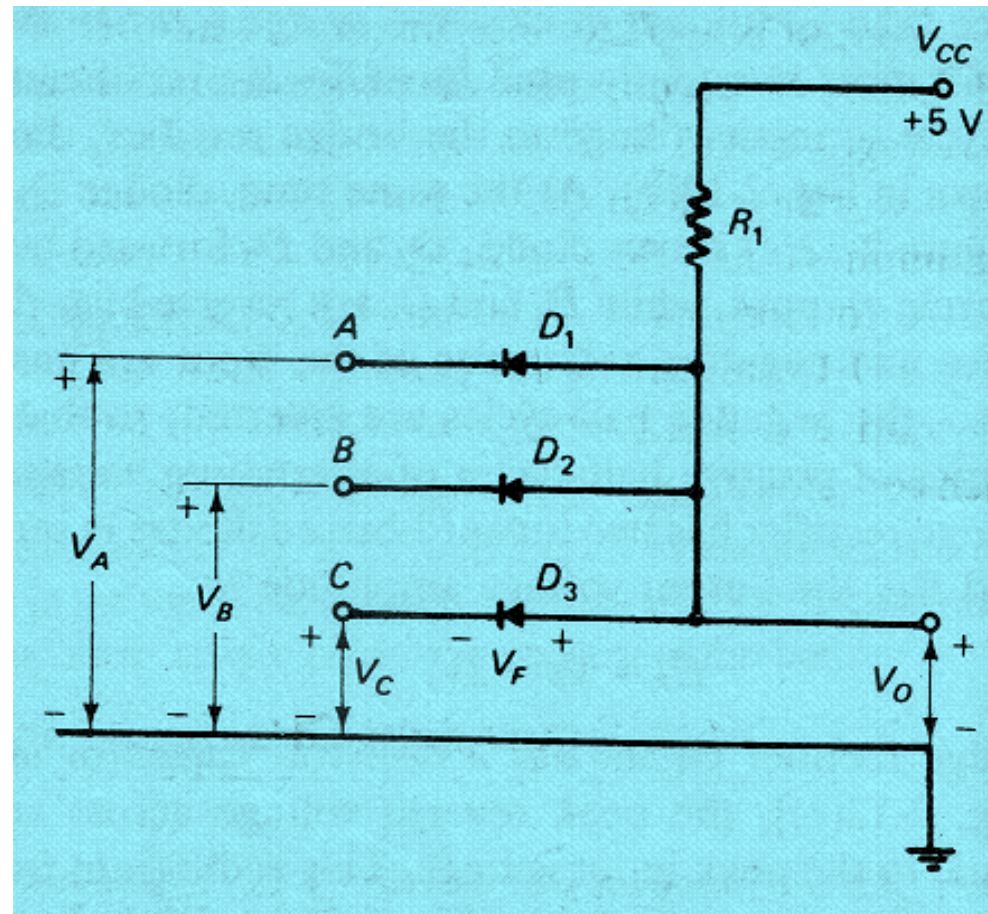


Diode Logic Circuits


OR Logic

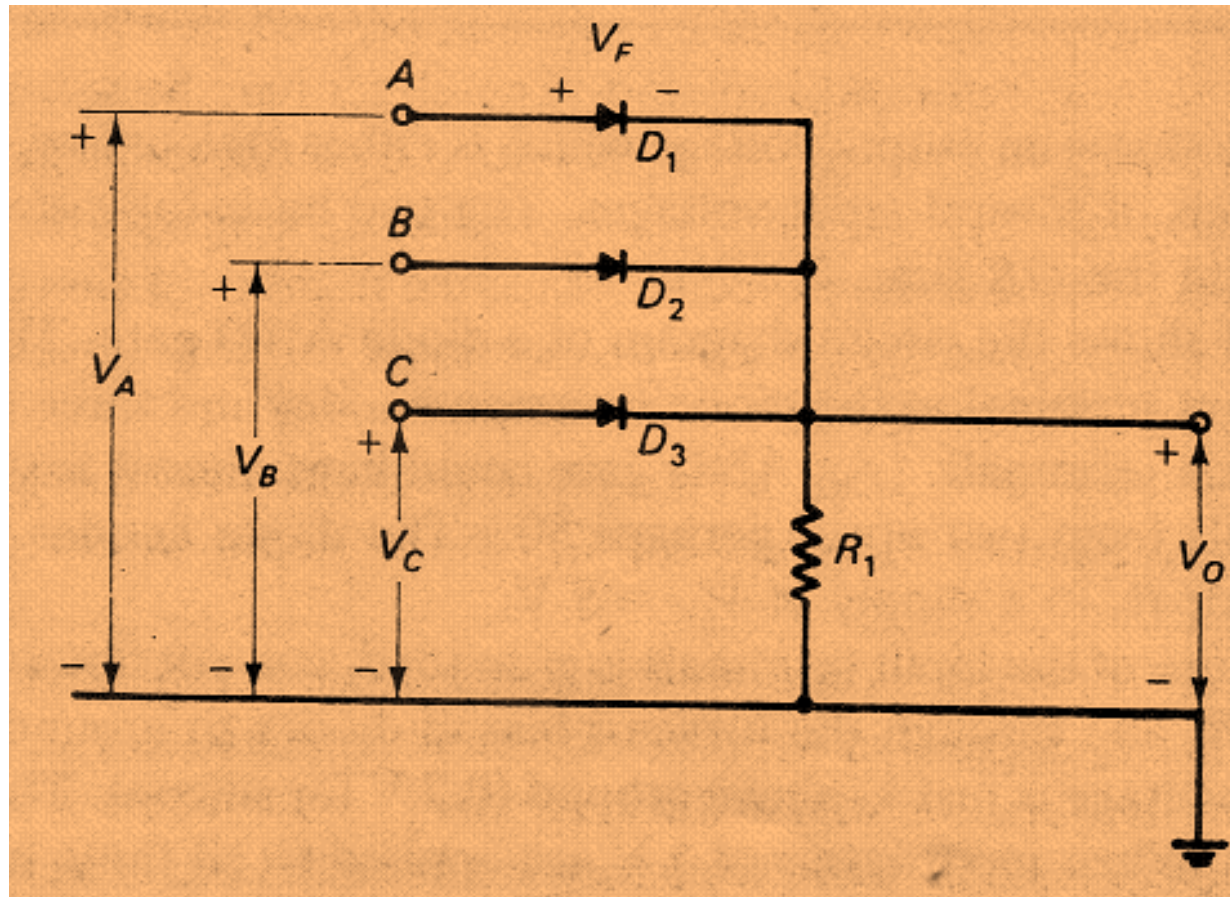

Diode Clipping and Clamping Circuits

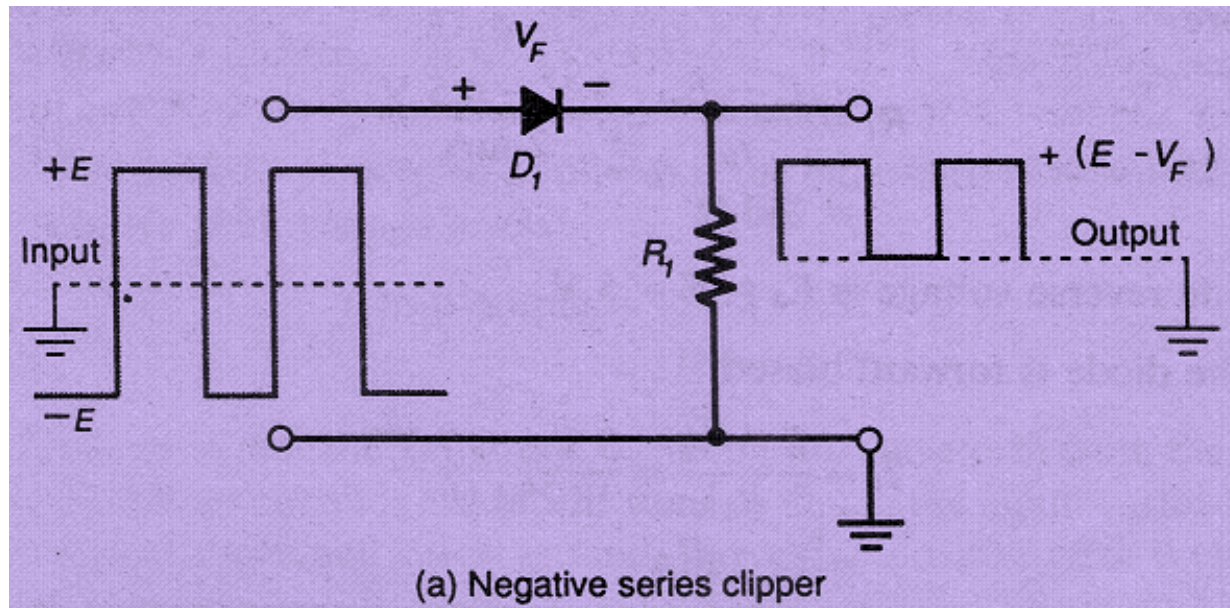

Diode Clipping and Clamping Circuits

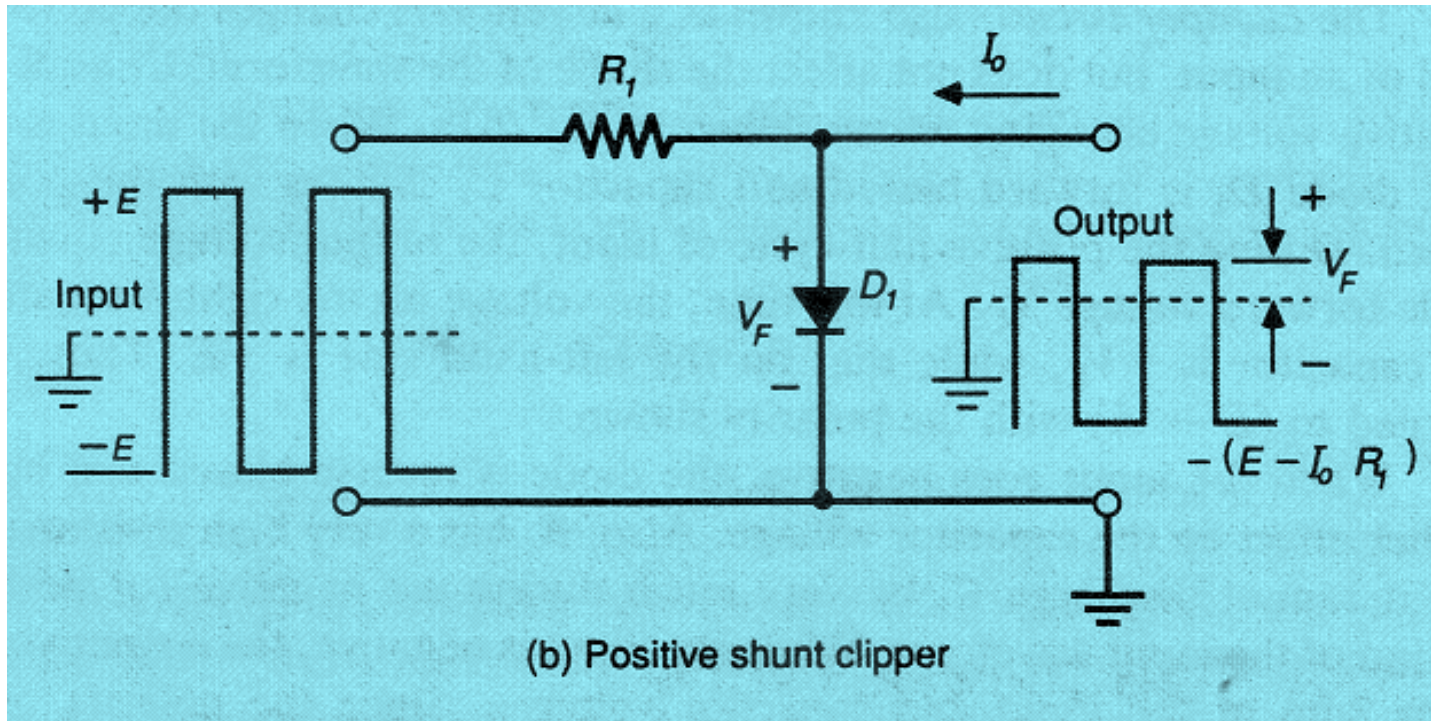

Diode Clipping and Clamping Circuits

A positive shunt clipper circuit has an input voltage of $E = \pm 5 \text{ V}$. The negative output voltage is to be -4.5 V when I_o is 2 mA . Determine the value of R_1 , and specify the diode forward current and reverse voltage.

When the diode is reverse biased,

$$E_o = E - I_o R_1$$

Therefore,


$$\begin{aligned} R_1 &= \frac{E - E_o}{I_o} = \frac{5 \text{ V} - 4.5 \text{ V}}{2 \text{ mA}} \\ &= 250 \Omega \end{aligned}$$

The diode reverse voltage is $E_R \approx E = 5 \text{ V}$.

When the diode is forward biased,

$$\begin{aligned} I_F &\approx \frac{E - V_F}{R_1} = \frac{5 \text{ V} - 0.7 \text{ V}}{250 \Omega} \\ &= 17.2 \text{ mA} \end{aligned}$$


Diode Clipping and Clamping Circuits

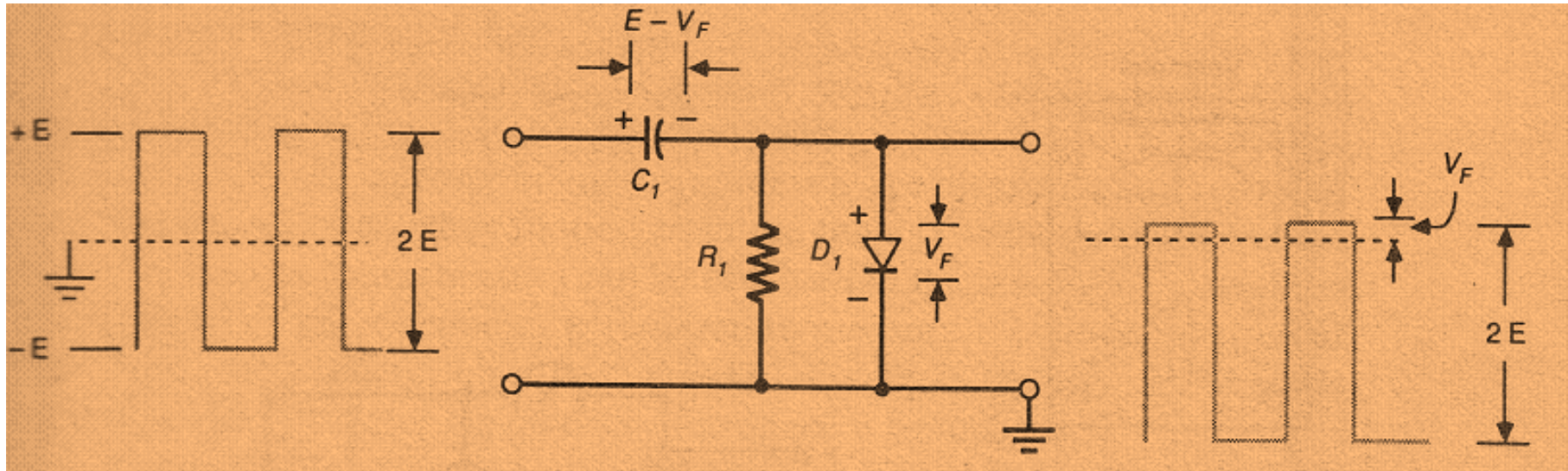

$$\begin{aligned} \text{Output} &= -E - (E - V_F) \\ &= -(2E - V_F) \end{aligned}$$

$$\begin{aligned} \text{p-to-p output} &= V_F - [-(2E - V_F)] \\ &= 2E \end{aligned}$$

Power Dissipation in Diodes

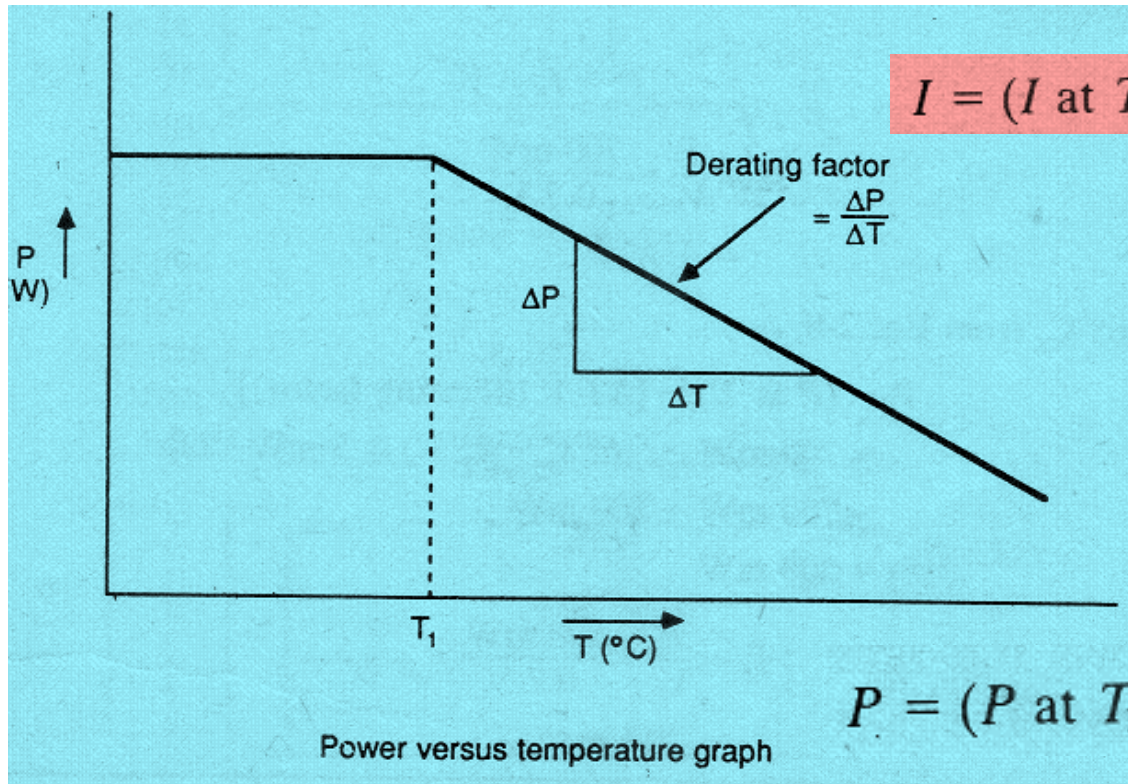

$$I = (I \text{ at } T_1) - [\Delta T \times (\text{derating factor})]$$

$$P = (P \text{ at } T_1) - [\Delta T \times (\text{derating factor})]$$

Or, Current vs. Temperature Graph!

Power Dissipation in Diodes

The maximum power that may be dissipated in a diode is listed on the data sheet as 700 mW at 25°C. The derating factor specified is 5 mW/°C. If the diode forward voltage drop is 0.7 V, calculate the maximum forward current that may be passed at 25°C and at 65°C.

At 25°C,

$$P = I_F \times V_F$$

or

$$I_F = \frac{P}{V_F} = \frac{700 \text{ mW}}{0.7 \text{ V}} \\ = 1 \text{ A}$$

At 65°C, from Eq. 2-8,

$$P = (P \text{ at } T_1) - [\Delta T \times (\text{derating factor})] \\ = 700 \text{ mW} - [(65^\circ\text{C} - 25^\circ\text{C}) \times 5 \text{ mW}/^\circ\text{C}] \\ = 700 \text{ mW} - 200 \text{ mW} \\ = 500 \text{ mW}$$

$$I_F = \frac{P}{V_F} = \frac{500 \text{ mW}}{0.7 \text{ V}}$$

Q & A

